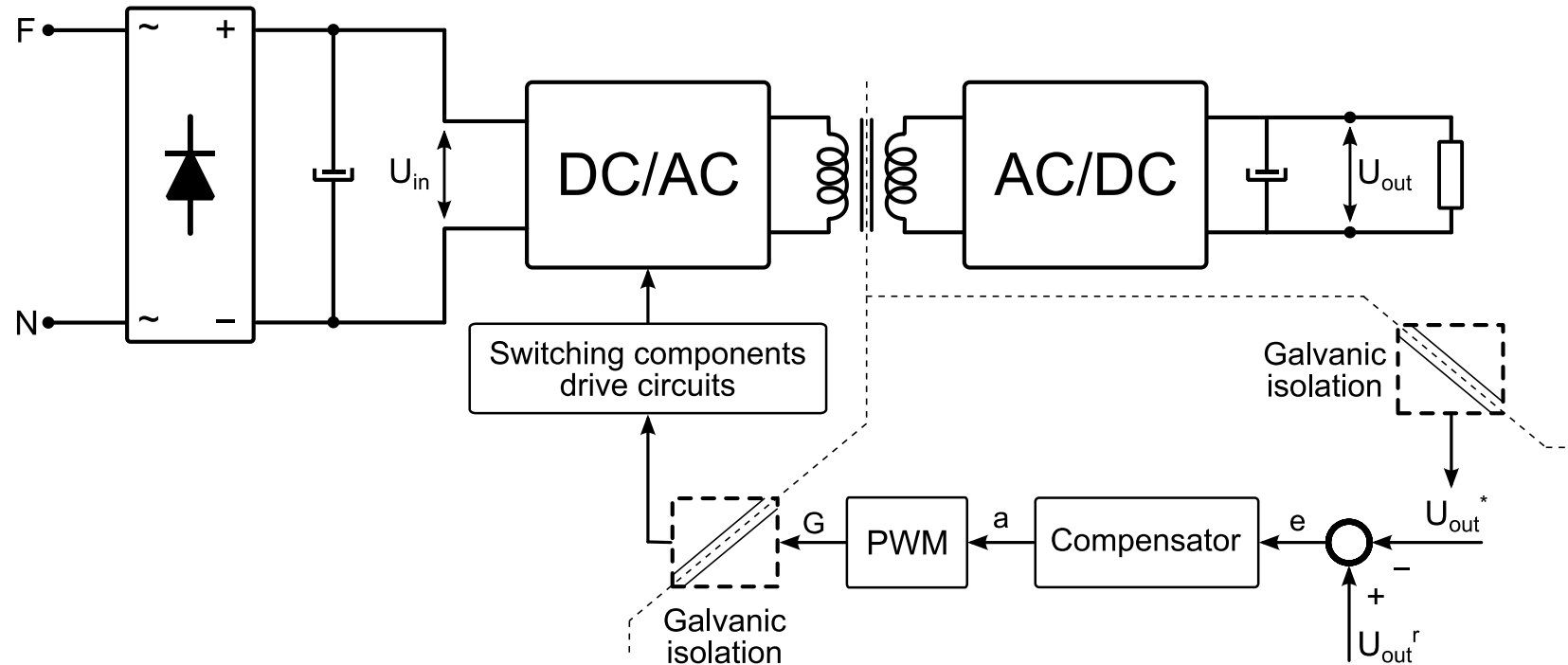


DC POWER SUPPLY

ISOLATED POWER SUPPLIES

DC POWER SUPPLY

Isolated (DC) power supplies - Concept



Galvanic isolation in control circuitry

- Electromagnetic (additional turn on HF transformer)
Optical (linear optocoupler)
- Electromagnetic (impulse transformer)
Optical (optocoupler)

DC POWER SUPPLY

Isolated (DC) power supplies - Concept

High-frequency transformer

- Transformer size

With the increase in (switching) frequency, the volume/size of the transformer decreases.


For the same maximum flux density, the higher the frequency, higher the transferred energy.

- Core materials

Ferrite (20kHz ÷ 1MHz)


- Core utilization

- DC excitation:

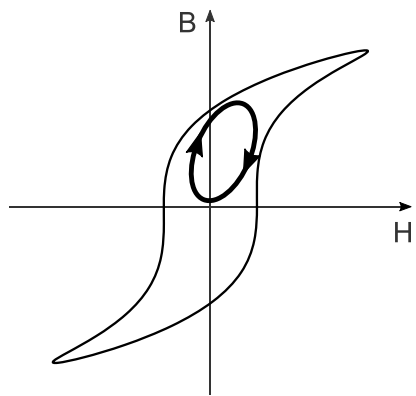


- Forward
- Flyback

- AC excitation:

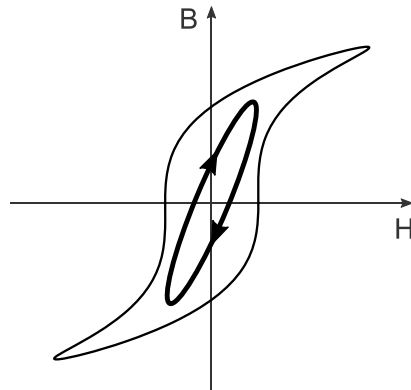


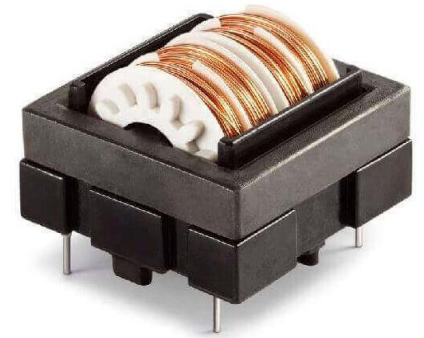
- Push-pull (symmetrical)
- Half-bridge
- Bridge



DC POWER SUPPLY

Isolated (DC) power supplies - Concept

High-frequency transformer



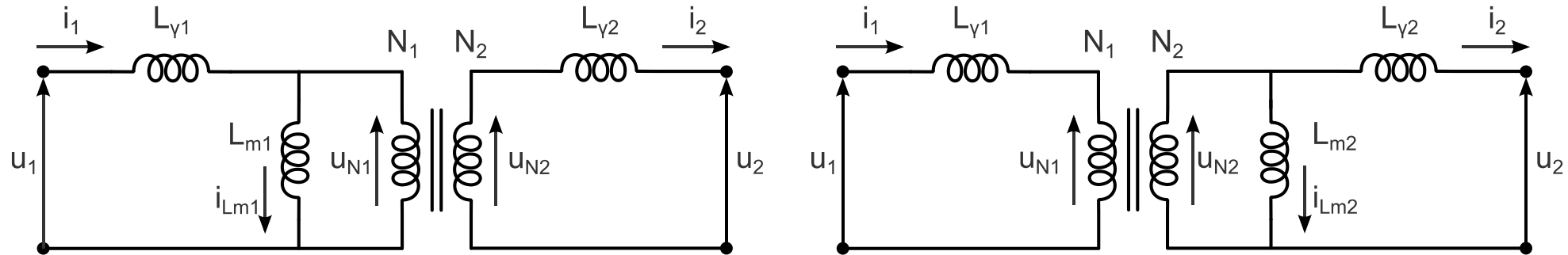
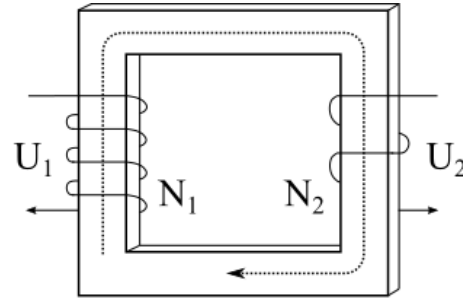


$$\frac{u_{N2}}{u_{N1}} = \frac{N_2}{N_1}$$

DC POWER SUPPLY

Isolated (DC) power supplies - Concept




High-frequency transformer

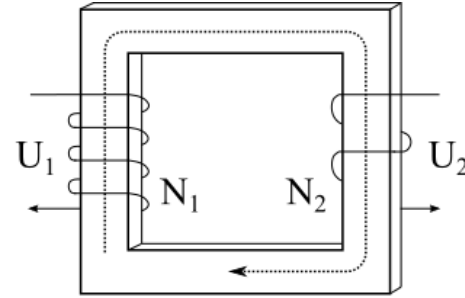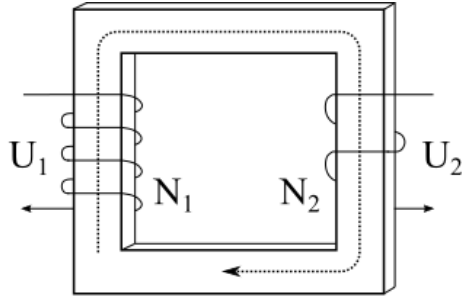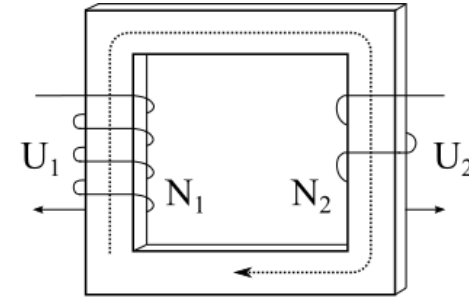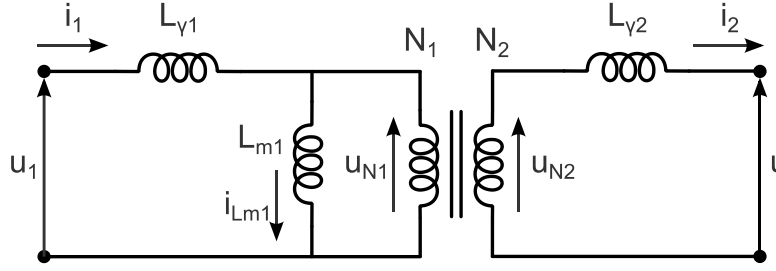

DC POWER SUPPLY

Isolated (DC) power supplies - Concept


Flyback (transformer)

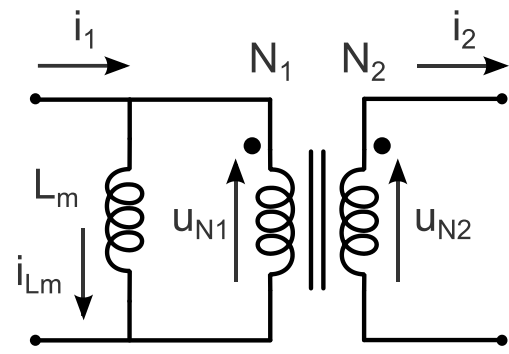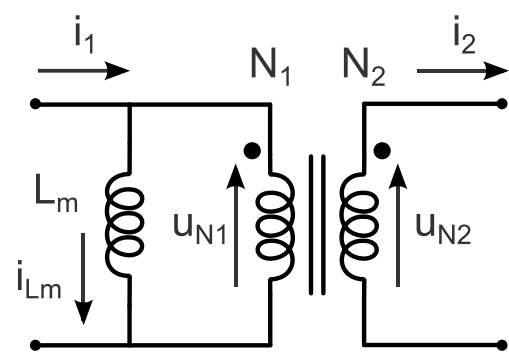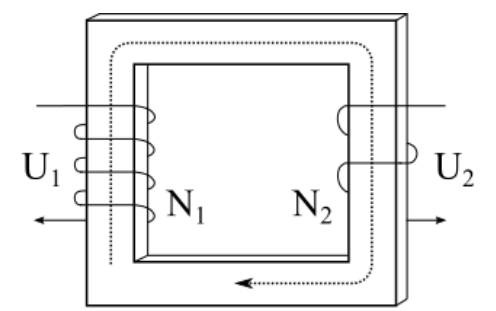

DC POWER SUPPLY

Isolated (DC) power supplies - Concept



Flyback (transformer)

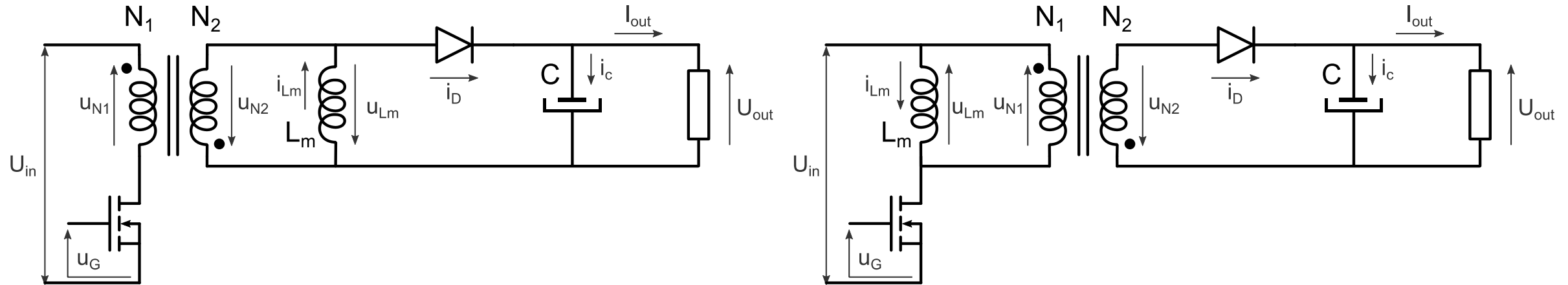

DC POWER SUPPLY

Isolated (DC) power supplies

Flyback converter

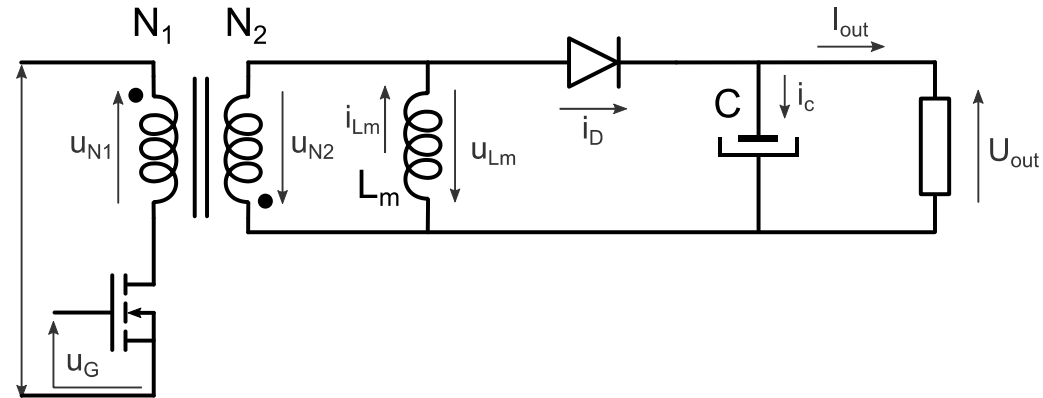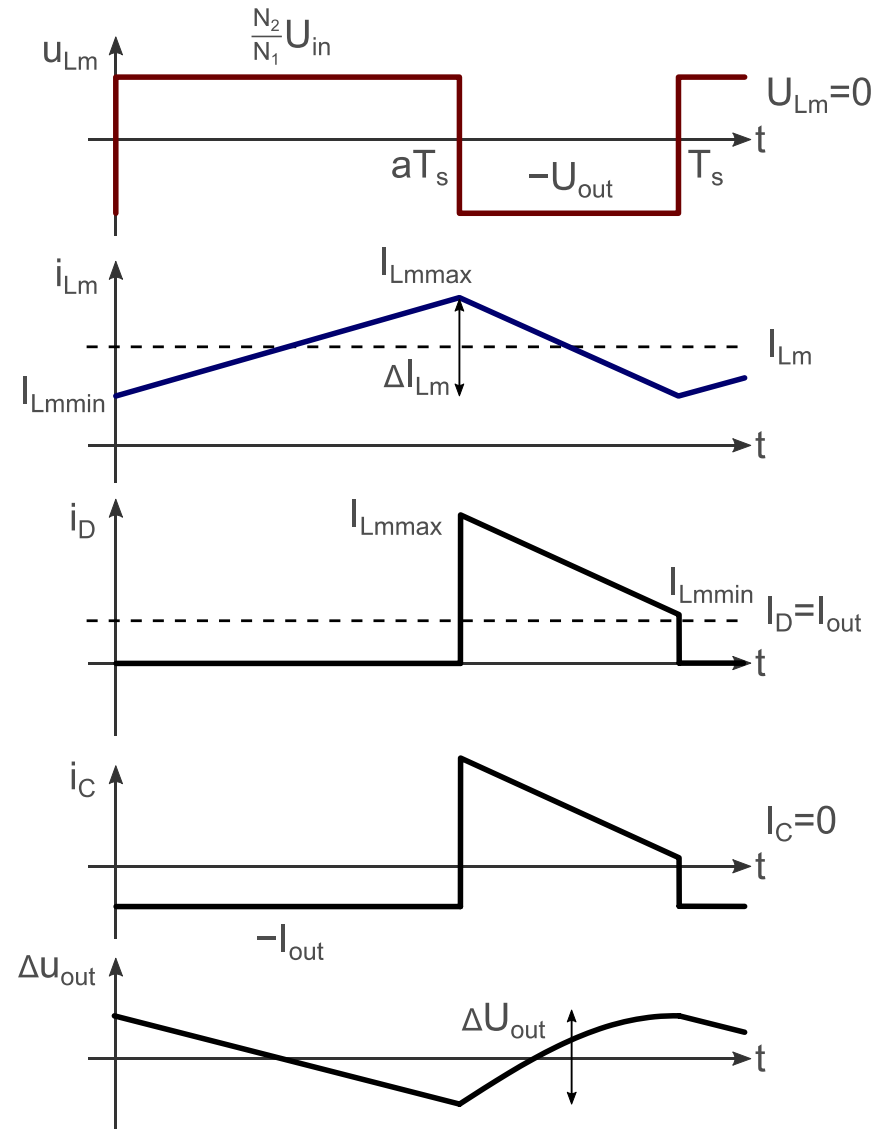

- Voltage “turns ratio”:



$$U_{Lm} = 0 \Rightarrow \frac{N_2}{N_1} U_{in} \cdot aT_s = U_{out} \cdot (1 - a)T_s$$

$$\frac{U_{out}}{U_{in}} = \frac{N_2}{N_1} \frac{a}{1 - a}$$

DC POWER SUPPLY

Isolated (DC) power supplies


Flyback converter

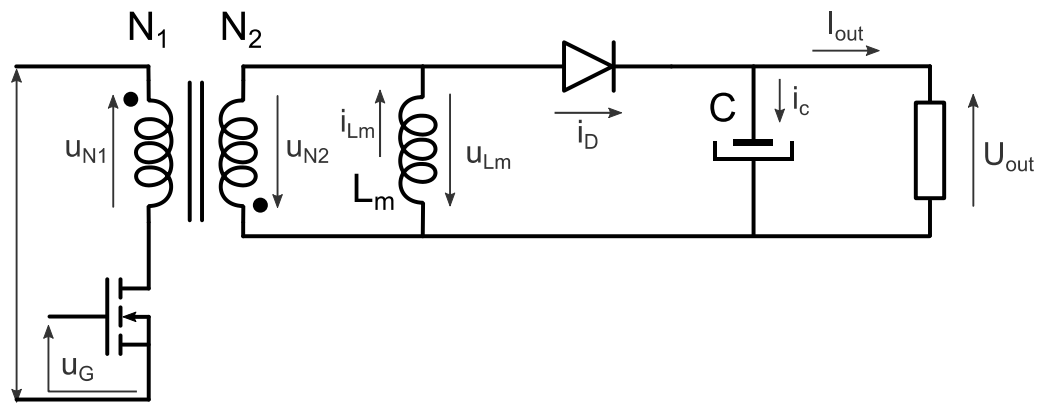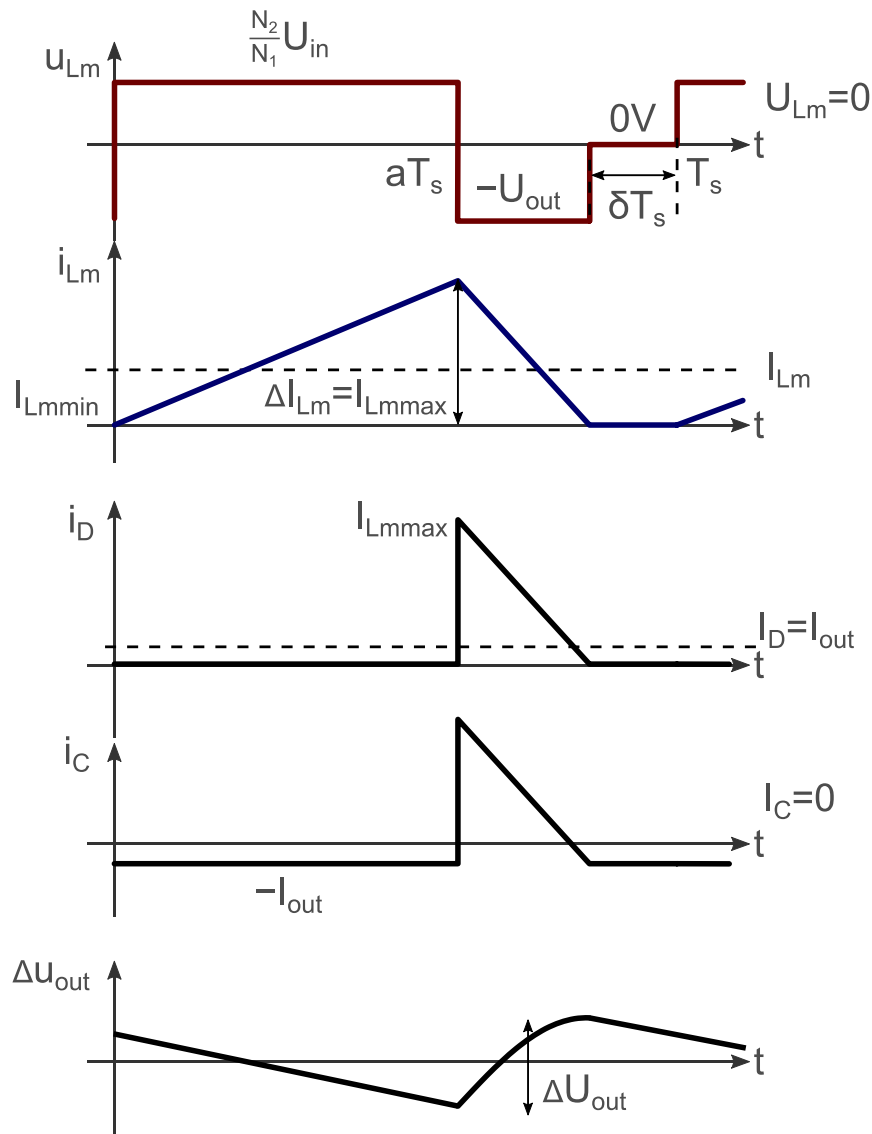

DC POWER SUPPLY

Isolated (DC) power supplies

Flyback converter

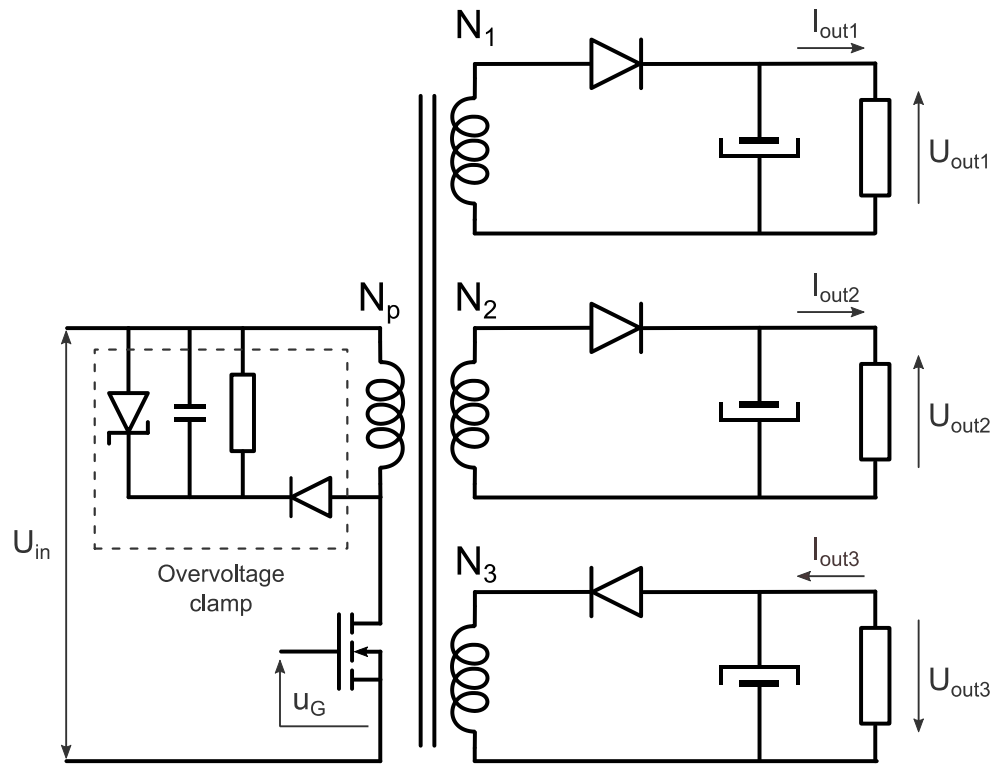

$$U_{out1} = \frac{N_1}{N_2} U_{out2} = \frac{N_1}{N_3} U_{out3}$$

