





ADDITIONAL NOTES

- Power quality issues.
- Application examples.
- Additional circuitry that secures proper rectifiers operation.

RECTIFIERS

Additional notes

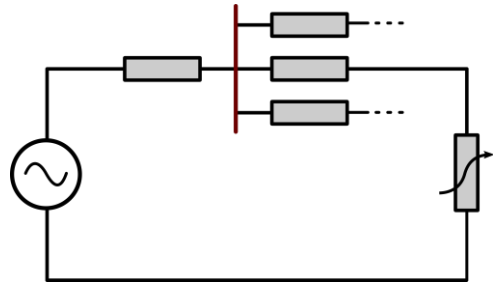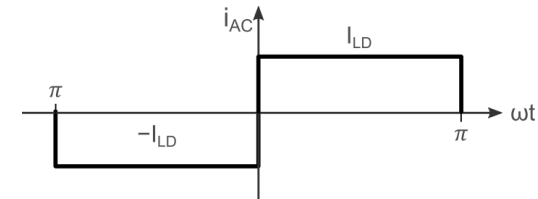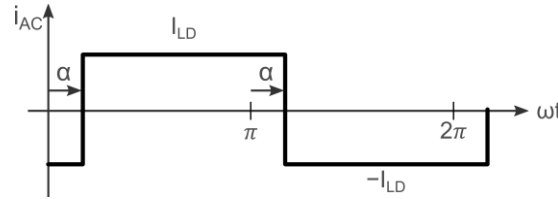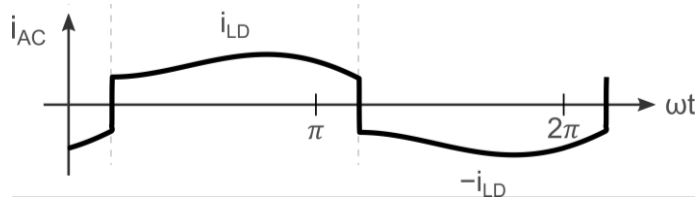Power quality issues (single-phase thyristor bridge):



Harmonic analysis:

$$x(\omega t) = A_0 + \sum_{h=1}^{\infty} [A_h \cdot \cos(h\omega t) + B_h \cdot \sin(h\omega t)]$$

$$A_h = \frac{1}{\pi} \int_{-\pi}^{\pi} i_{AC}(\omega t) \cdot \cos(h\omega t) \cdot d(\omega t),$$

$$B_h = \frac{1}{\pi} \int_{-\pi}^{\pi} i_{AC}(\omega t) \cdot \sin(h\omega t) \cdot d(\omega t).$$


$$I_{ACrms} =$$

$$i_{AC} = ?$$

RECTIFIERS



Additional notes

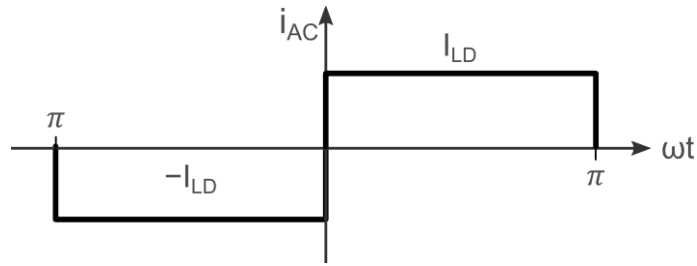Power quality issues (single-phase thyristor bridge) - harmonics:



$$A_h = \frac{1}{\pi} \int_{-\pi}^{\pi} i_{AC}(\omega t) \cdot \cos(h\omega t) \cdot d(\omega t) \quad A_h = 0$$
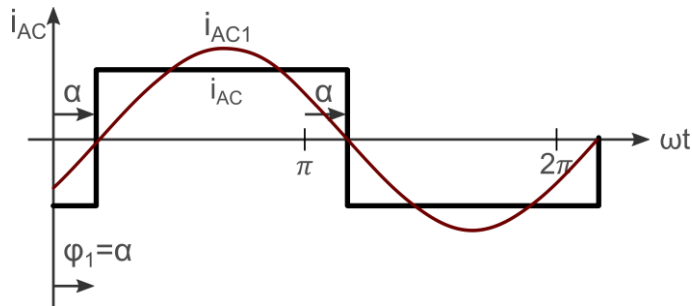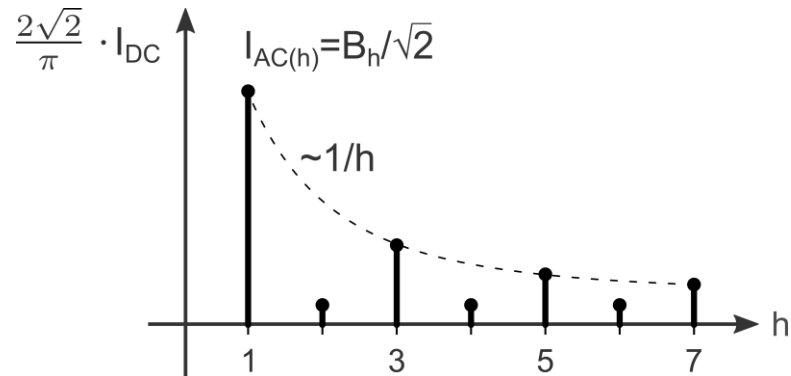
$$B_h = \frac{1}{\pi} \int_{-\pi}^{\pi} i_{AC}(\omega t) \cdot \sin(h\omega t) \cdot d(\omega t)$$




$$x(\omega t) = A_0 + \sum_{h=1}^{\infty} [A_h \cdot \cos(h\omega t) + B_h \cdot \sin(h\omega t)]$$

RECTIFIERS

Additional notes

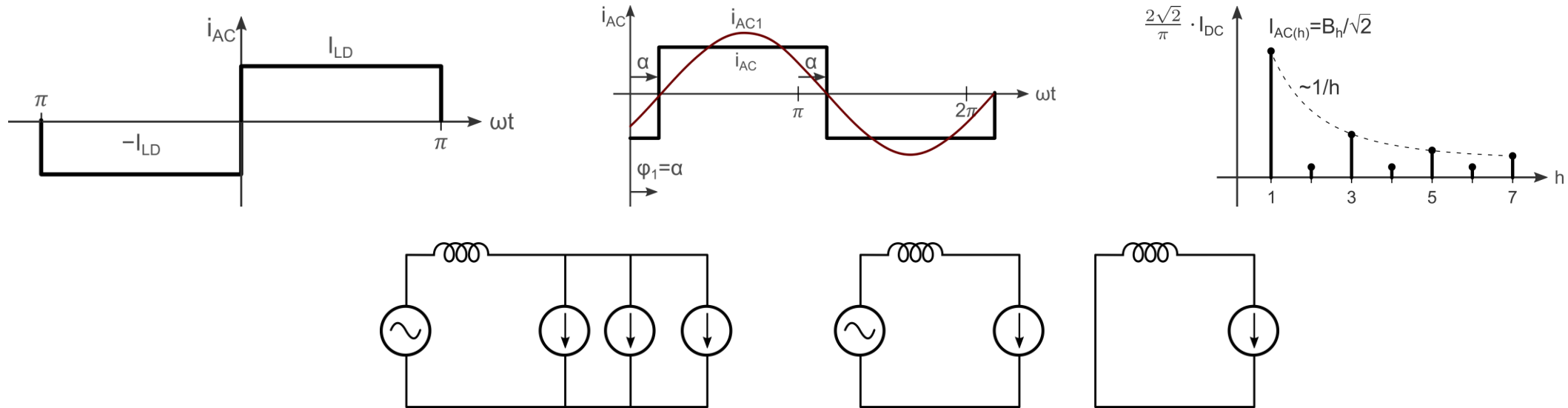Power quality issues (single-phase thyristor bridge) - harmonics:







def.: $P_{AC} =$

def.: $Q_{AC} =$

RECTIFIERS

Additional notes

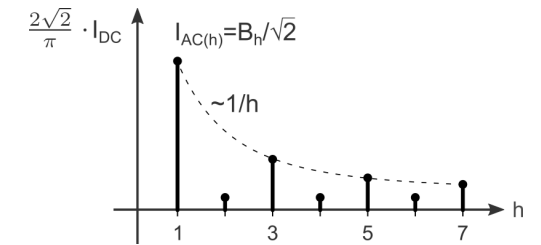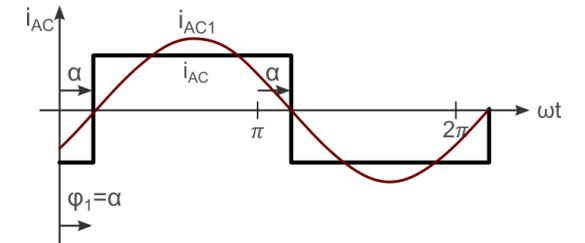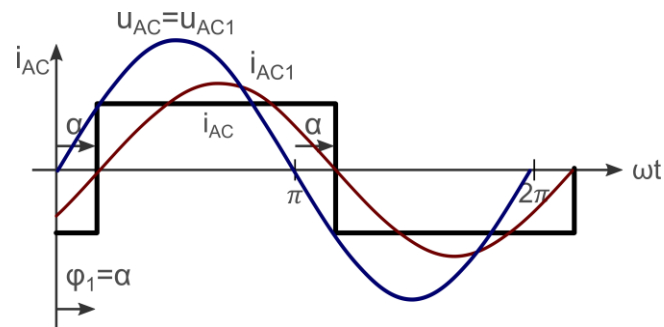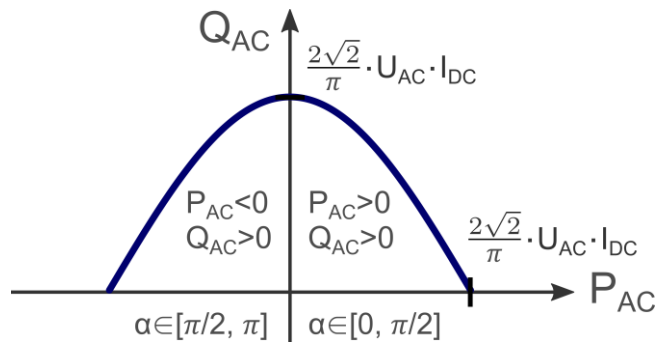
Power quality issues (single-phase thyristor bridge) - harmonics:



RECTIFIERS

Additional notes



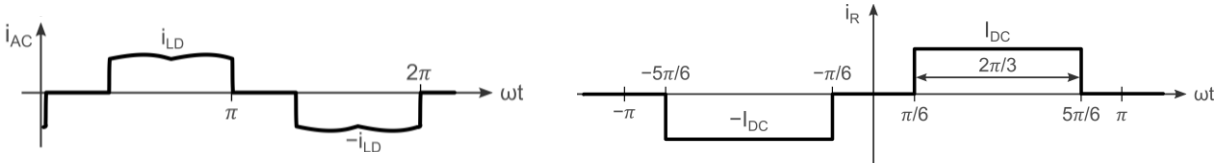
Power quality issues (three-phase thyristor bridge) - harmonics:



$I_{ACrms} =$

$P_{AC} =$



$Q_{AC} =$

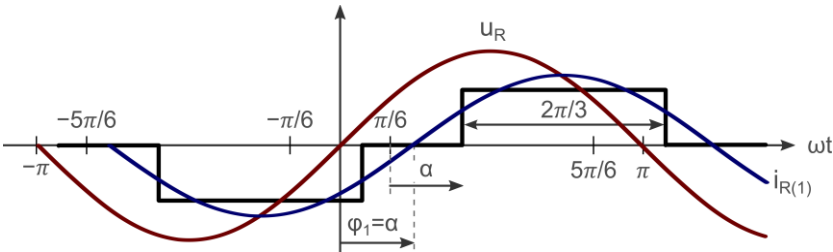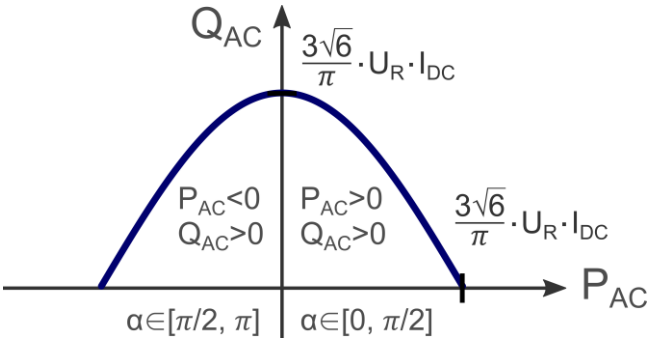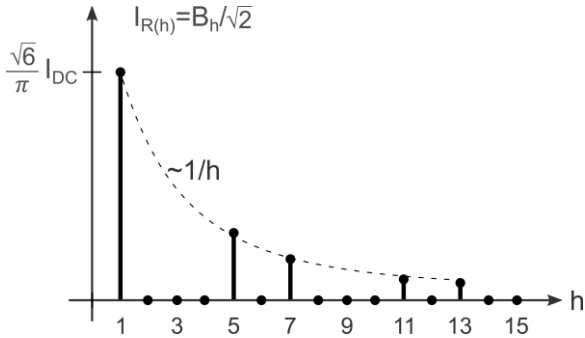

RECTIFIERS

Additional notes





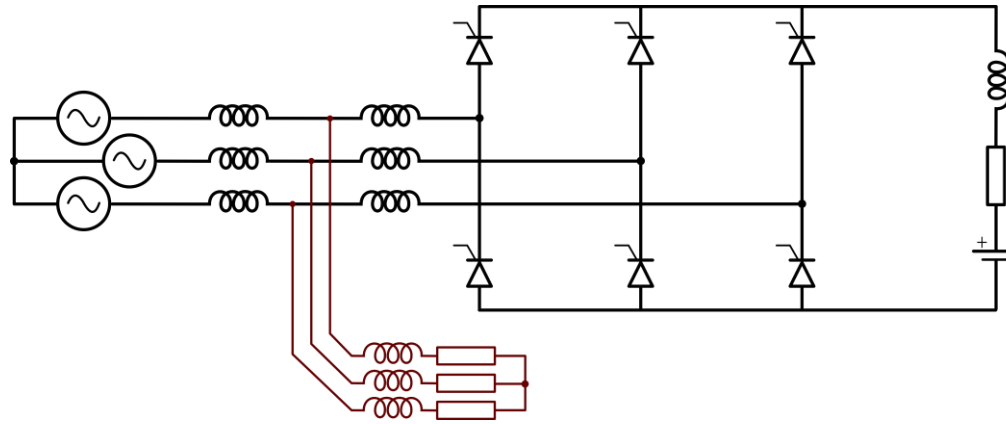
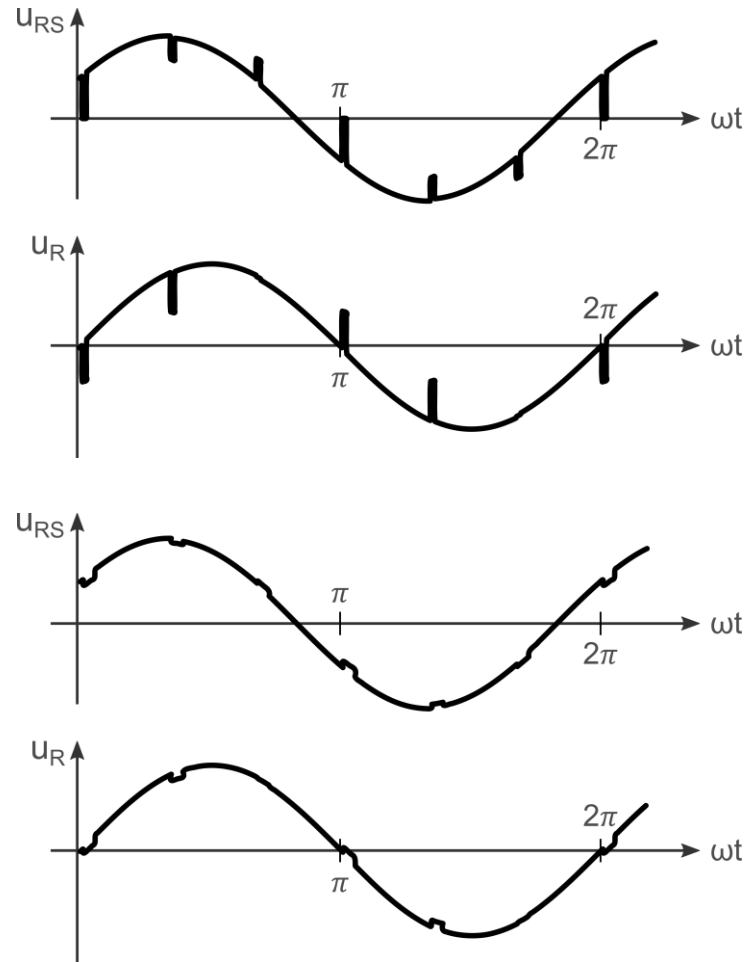
Power quality issues (thyristor bridges) -
voltage deviations:



RECTIFIERS

Additional notes

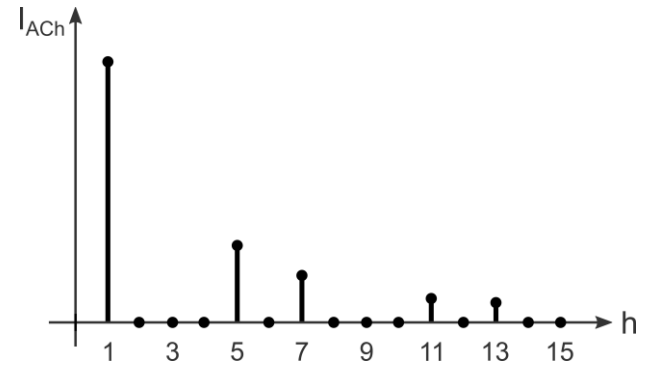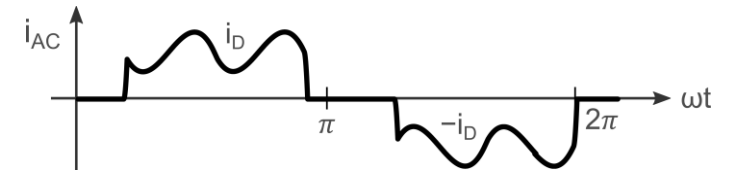
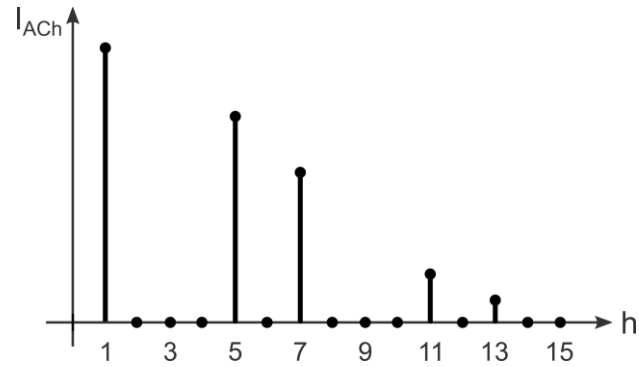
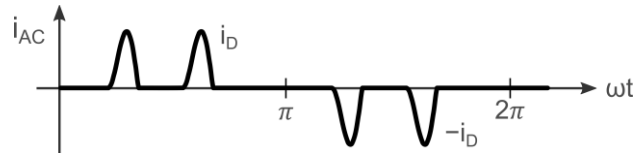
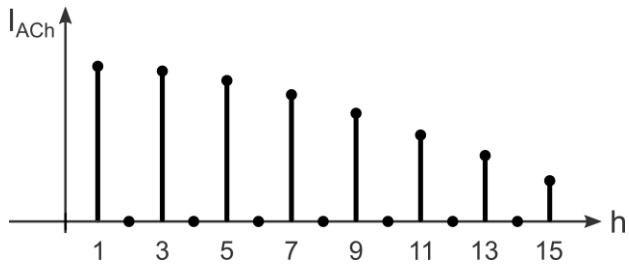
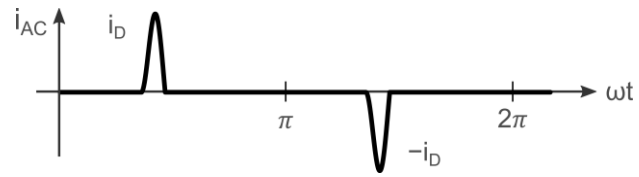
Power quality issues (diode bridges) - harmonics :



RECTIFIERS

Additional notes

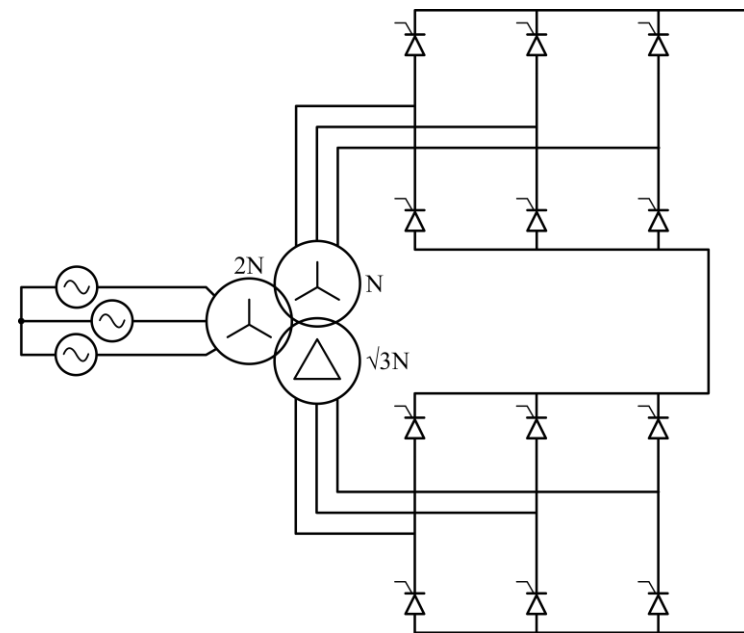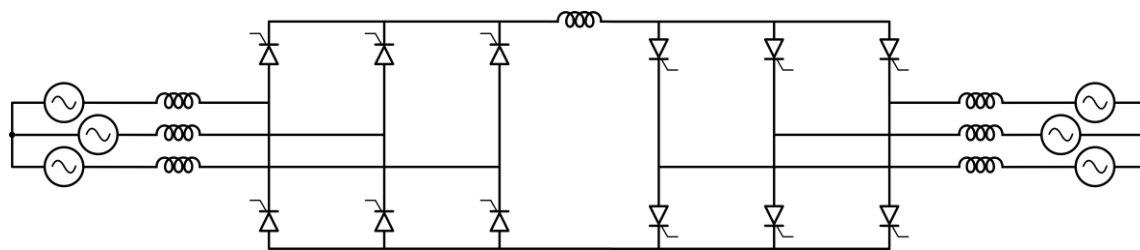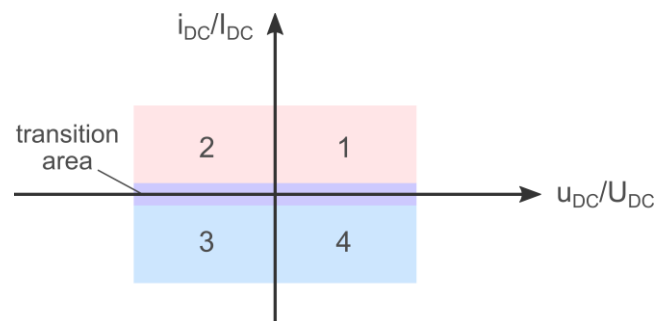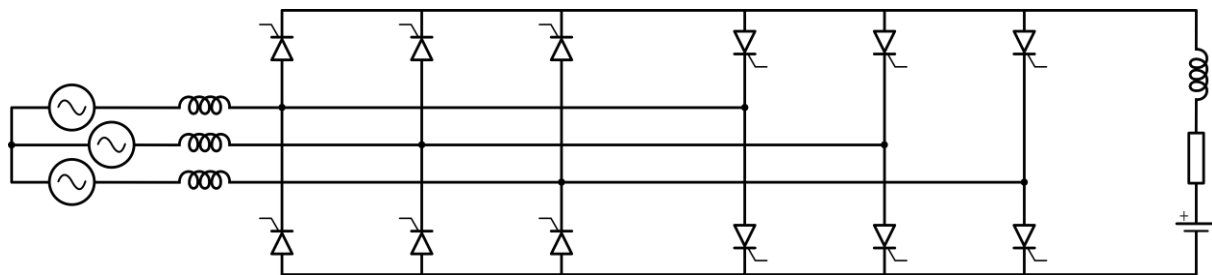
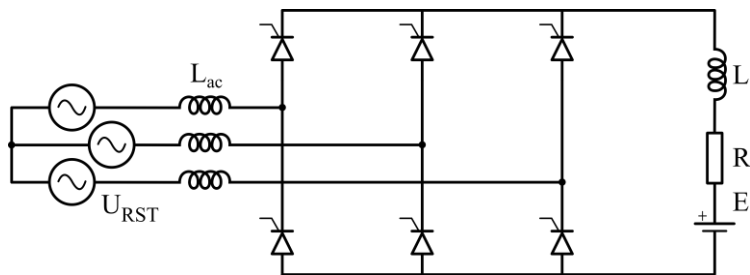
Thyristor bridges - application examples:



RECTIFIERS

Additional notes

Diode bridges - application example:

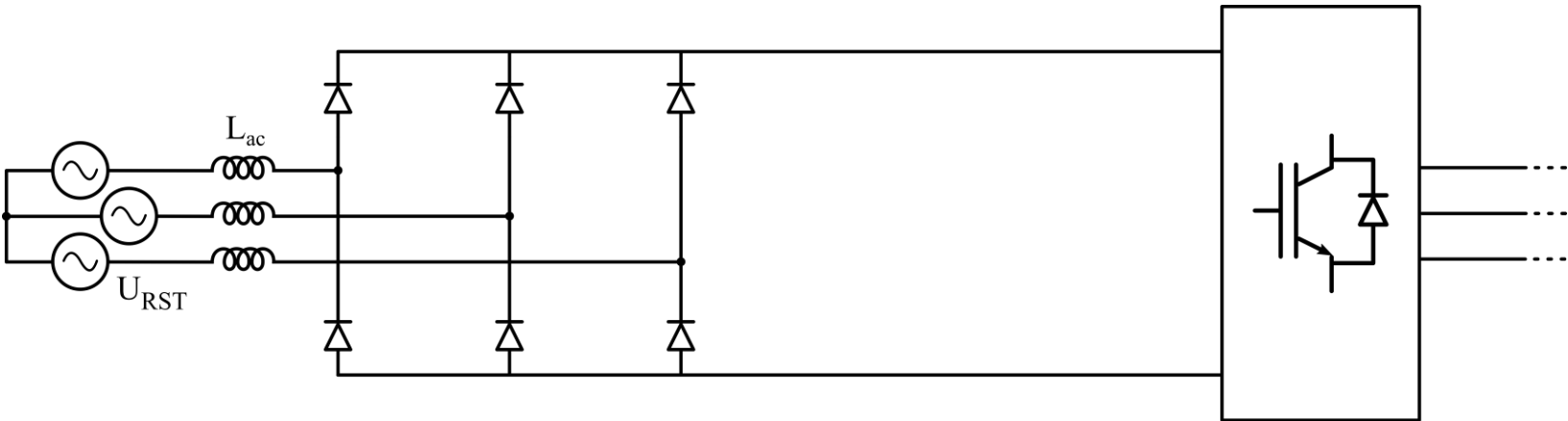
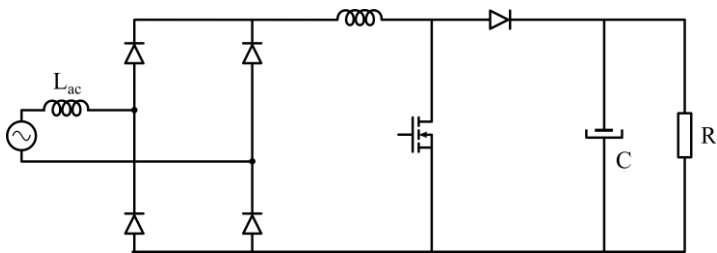


Additional circuitry that secures proper rectifiers operation:

RECTIFIERS

Additional notes

Thyristor bridges - synchronization:

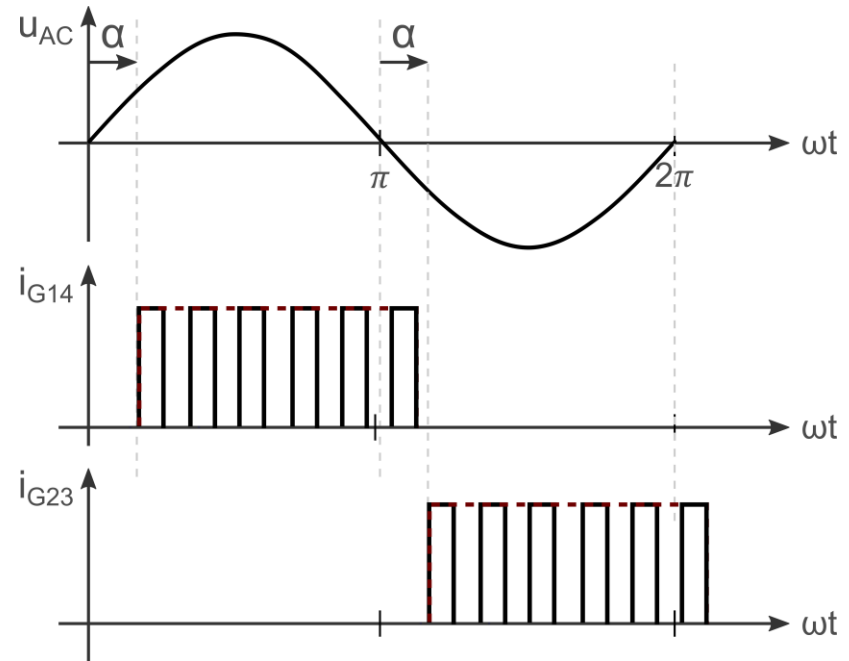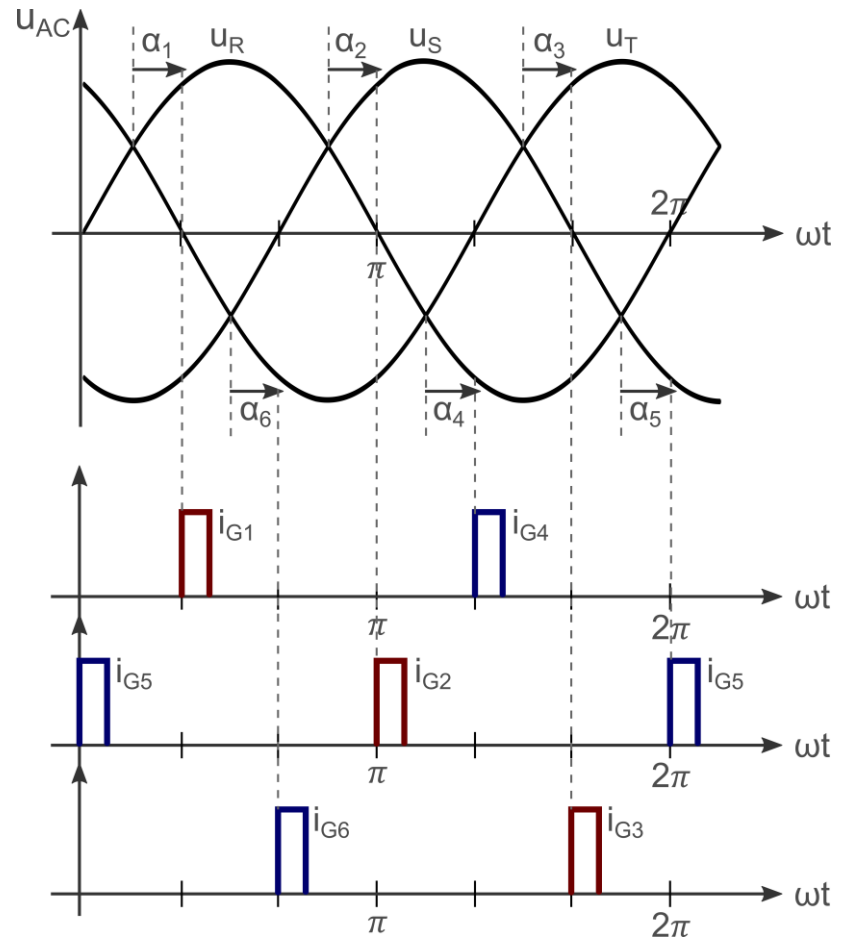

RECTIFIERS

Additional notes

- Harmonic analysis is of particular importance when addressing rectifiers,
- The rectifiers (can) cause significant power quality problems,
- Additional filtering can be used to mitigate power quality problems,
- Thyristor rectifiers generally consume reactive power,
- Both diode and thyristor bridges have large applicability,
- Diode bridges necessitate additional circuitry to operate safely,
- Thyristor bridges necessitate a continuous gate current or a train of gate current pulses if discontinuous operating mode (can) happen.

