


RECTIFIERS

THREE-PHASE RECTIFIERS

- Three-phase diode rectifiers.
- Three-phase thyristor rectifiers.

RECTIFIERS

Diode vs thyristor rectifiers


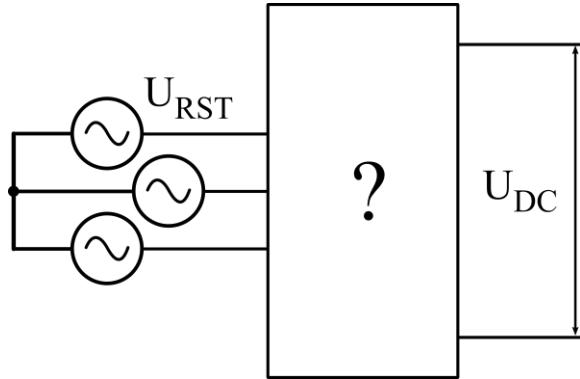


These rectifiers provide “either” small ΔU_{DC} “or” small ΔI_{DC} .

Types of three-phase rectifiers:

Uncontrolled vs Controlled (vs Half/semi-controlled)

Half-wave vs Full-wave

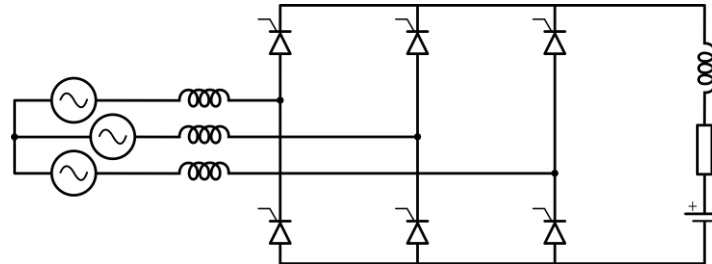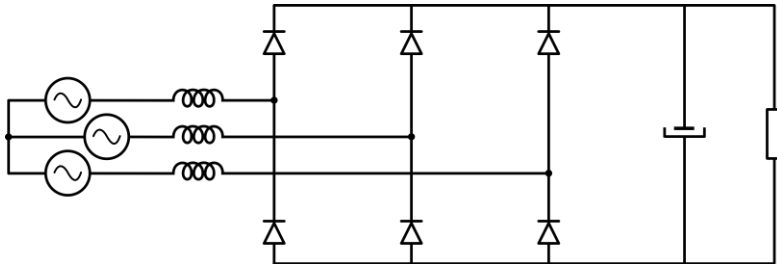

RECTIFIERS

Three-phase diode (uncontrolled) rectifier



$$U_{LDmax} = \sqrt{2} \cdot U_L$$

$$u_{-N} \approx u_R \quad u_{+N} \approx u_S$$

$$u_{LD} = u_{+N} - u_{-N} \approx u_{RS}$$

$$i_R = i_{LD}, \quad i_S = -i_{LD}$$

$$i_C = i_D - i_{LD},$$

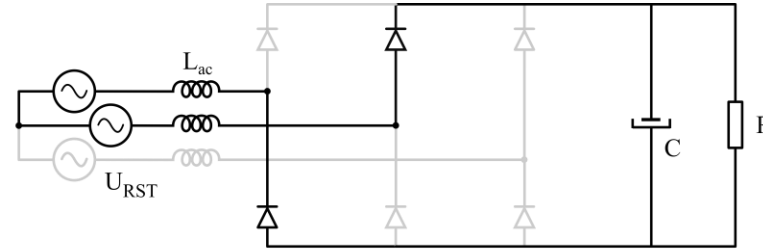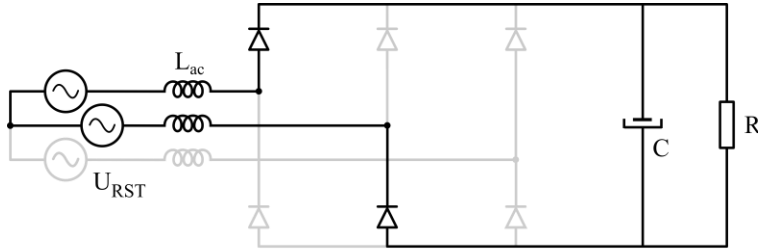

$$u_{-N} \approx \quad u_{+N} \approx$$

$$u_{LD} =$$

$$i_R = \quad i_S =$$



$$i_C =$$

$$u_{-N} \approx \quad u_{+N} \approx$$

$$u_{LD} =$$

$$i_R = \quad i_S =$$

$$i_C =$$

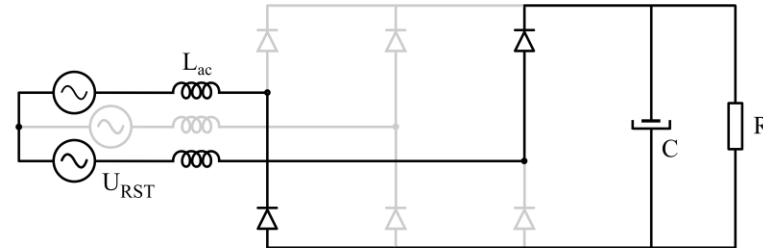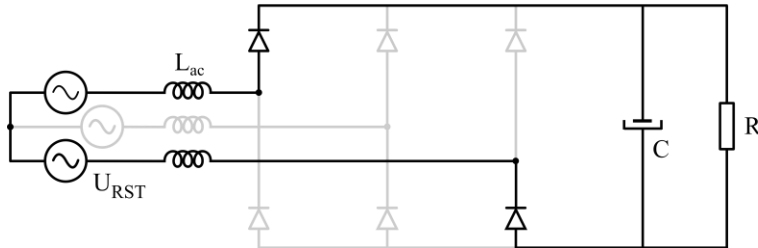

$$u_{-N} \approx \quad u_{+N} \approx$$

$$u_{LD} =$$


$$i_R = \quad i_S =$$

$$i_C =$$

$$u_{LD} \approx U_{LDmax} \cdot e^{-\frac{\omega t - \frac{\pi}{2}}{\omega \cdot \tau_{LD}}}, \quad \tau_{LD} = C \cdot R$$




$$i_R = 0A$$

$$i_C = -i_{LD}$$

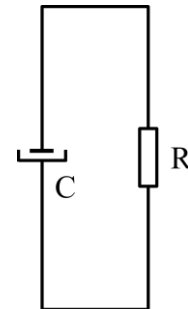

RECTIFIERS

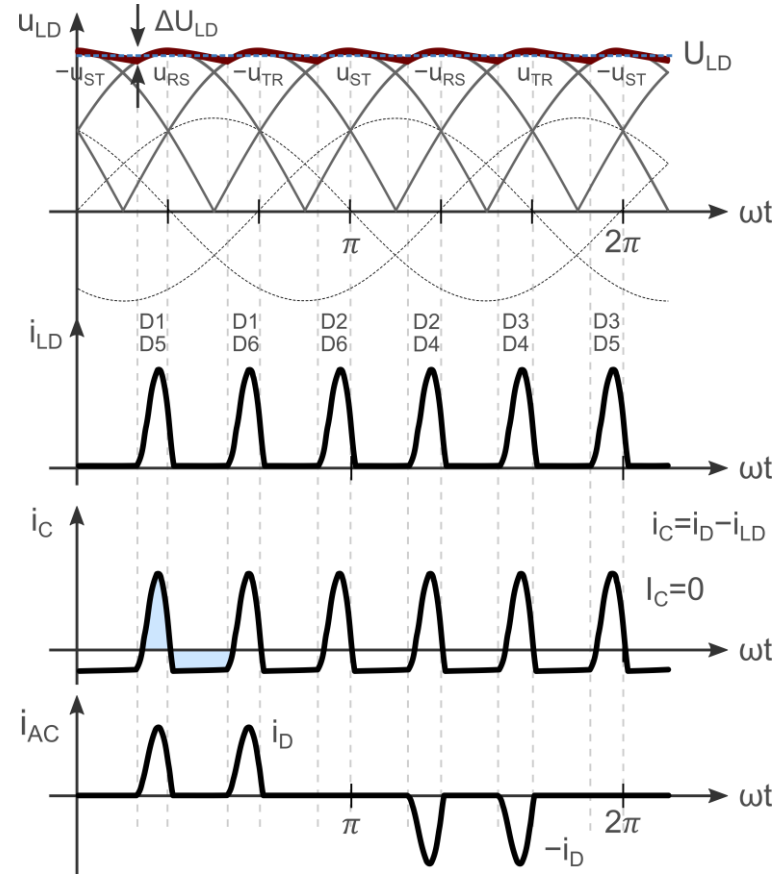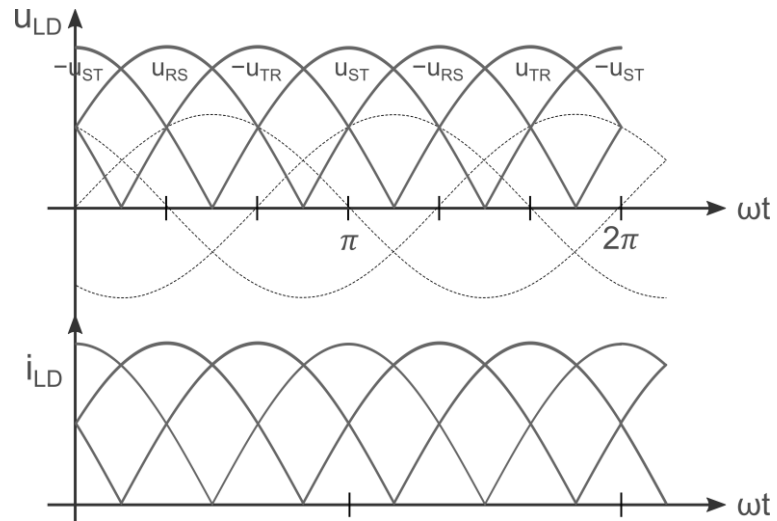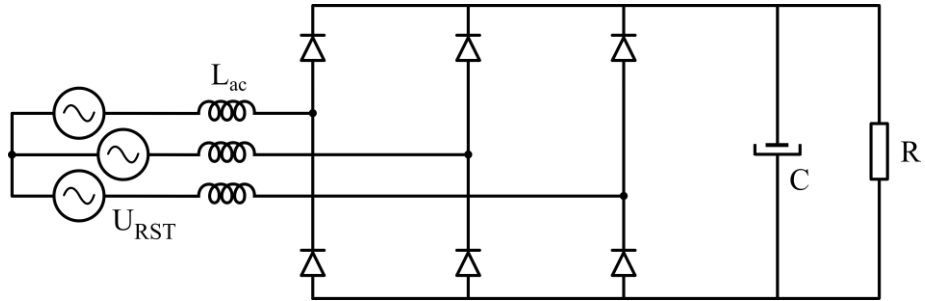
Three-phase diode (uncontrolled) rectifier



RECTIFIERS

Three-phase diode (uncontrolled) rectifier

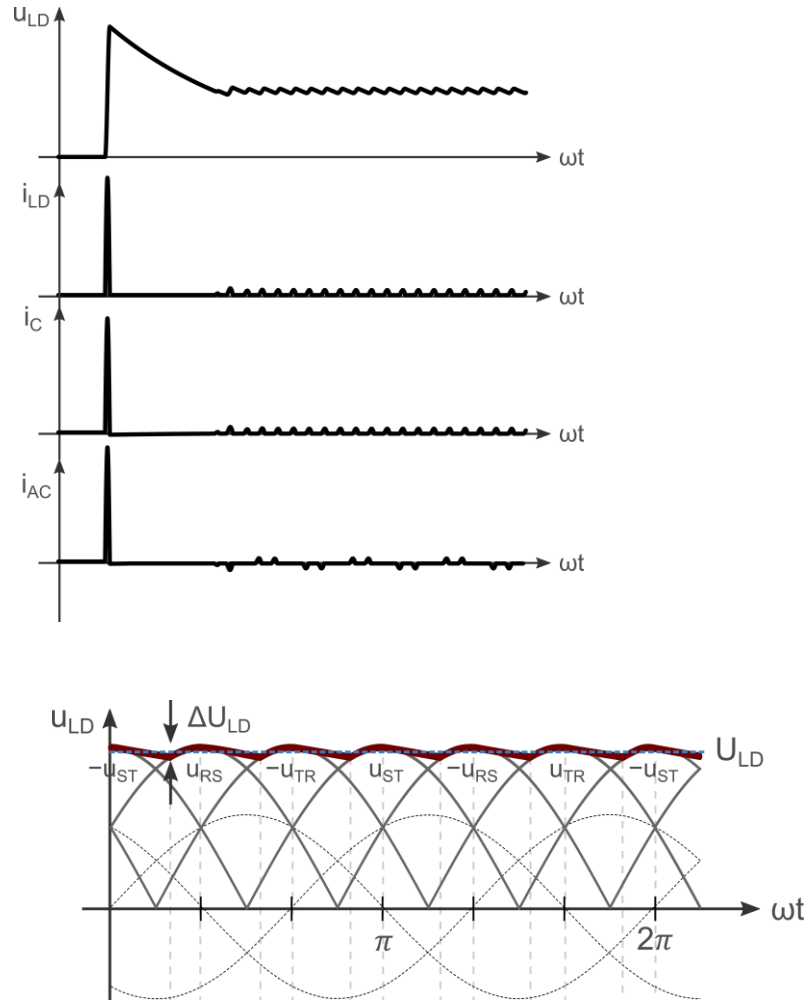Direct start with a discharged capacitor:



Capacitor sizing:

Assumption - $\Delta U_{LD} \ll U_{LD}$ ($\Delta U_{LD} \approx 0$)

$\Rightarrow i_{LD} \approx I_{LD}$ and the discharge time is (whole) 10/3 ms.

$$\Rightarrow \Delta U_{LDmax} = \frac{Q}{C} = \frac{I_{DC} \cdot \frac{10}{3} ms}{C} \text{ or } C = \frac{I_{DC} \cdot \frac{10}{3} ms}{\Delta U_{LD}}$$

Example:

$$U_{ACL} = 400V (50Hz), P_{LD} = 5kW, \Delta U_{LDmax} \leq 10\% \cdot U_{LD}$$

$$U_{LD} \approx U_{LDmax} = \sqrt{2} \cdot U_L = \sqrt{2} \cdot 400 = 566V$$

$$I_{LD} = \frac{5kW}{566V} = 8.84A, \Delta U_{DC} = 57V$$

$$C = \frac{8.84 \cdot 3.33ms}{57} = 516\mu F$$

RECTIFIERS

Three-phase thyristor (controlled) rectifier



$$L \gg L_{AC} \Rightarrow u_{LAC} \ll$$

$$u_{+N} \approx u_R$$

$$u_{-N} \approx u_S$$

$$u_{LD} = u_{+N} - u_{-N} \approx u_{RS}$$

$$i_R = i_{LD}, i_S = -i_{LD}$$

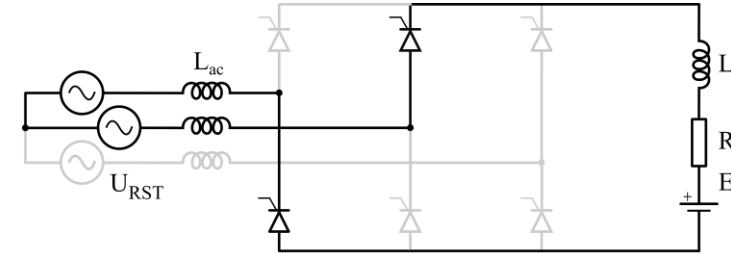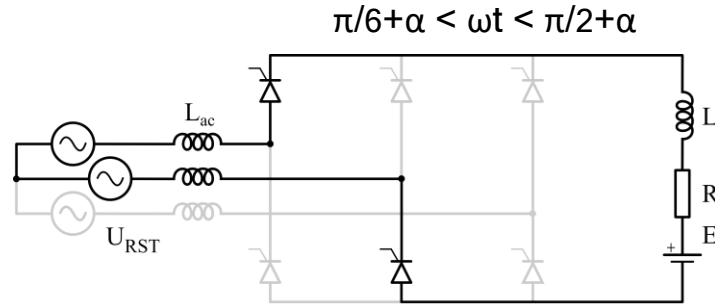

$$u_{+N} \approx$$

$$u_{-N} \approx$$

$$u_{LD} =$$



$$i_R =$$

$$u_{+N} \approx$$

$$u_{-N} \approx$$

$$u_{LD} =$$

$$i_R =$$

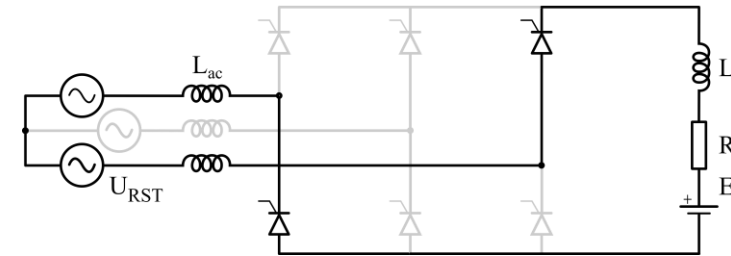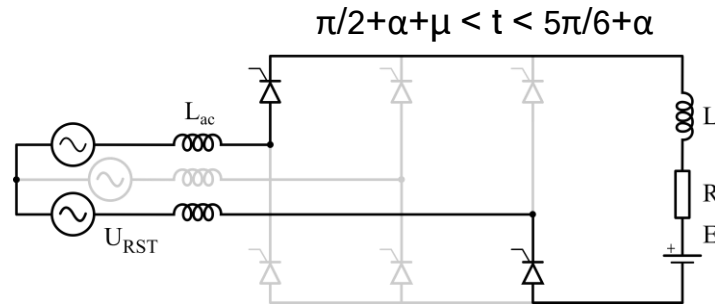

$$u_{+N} \approx$$

$$u_{-N} \approx$$

$$u_{LD} =$$


$$i_R =$$

$$u_{+N} \approx u_R$$

$$u_{-N} \approx u_S - u_{ST}/2$$





$$u_{LD} = u_{RS} + u_{ST}/2$$

$$i_R = i_{LD}$$

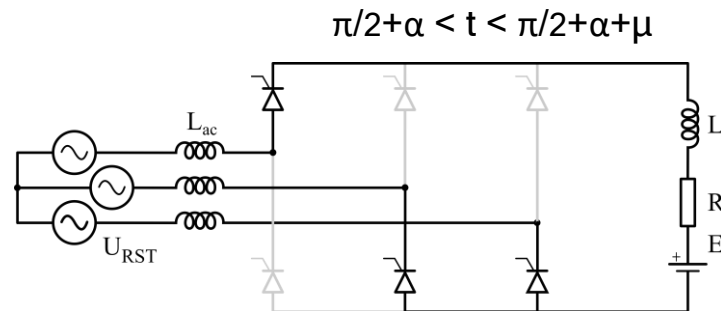

RECTIFIERS

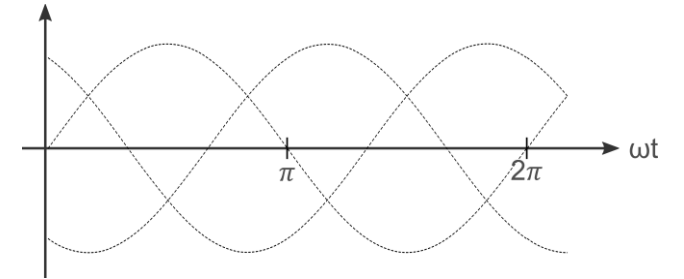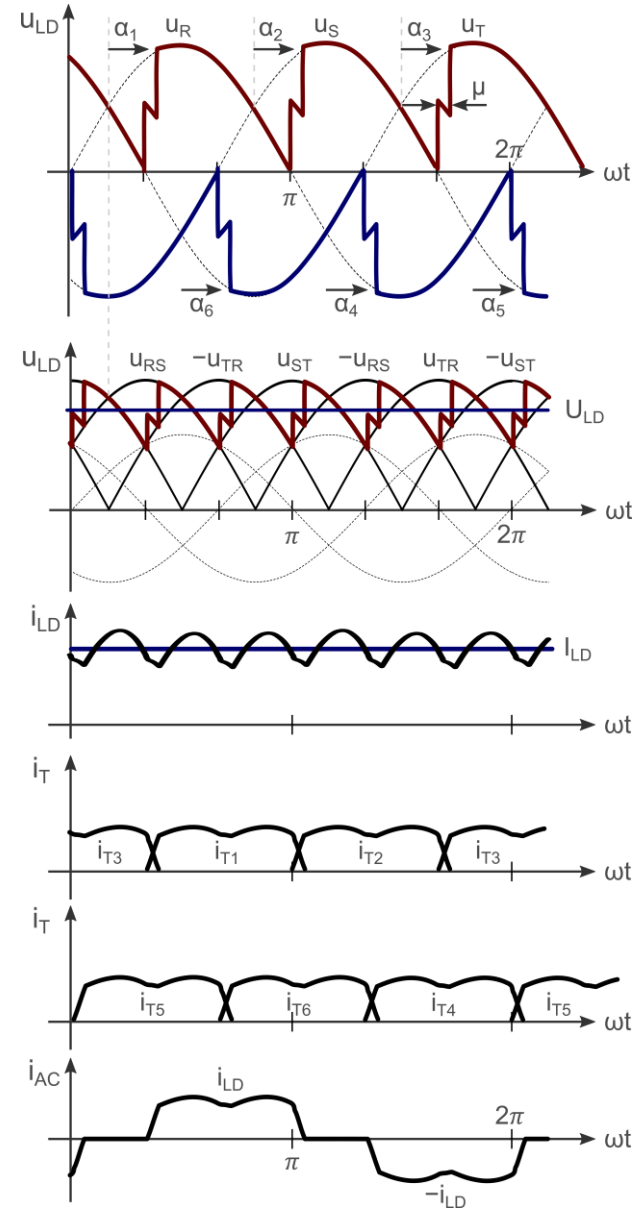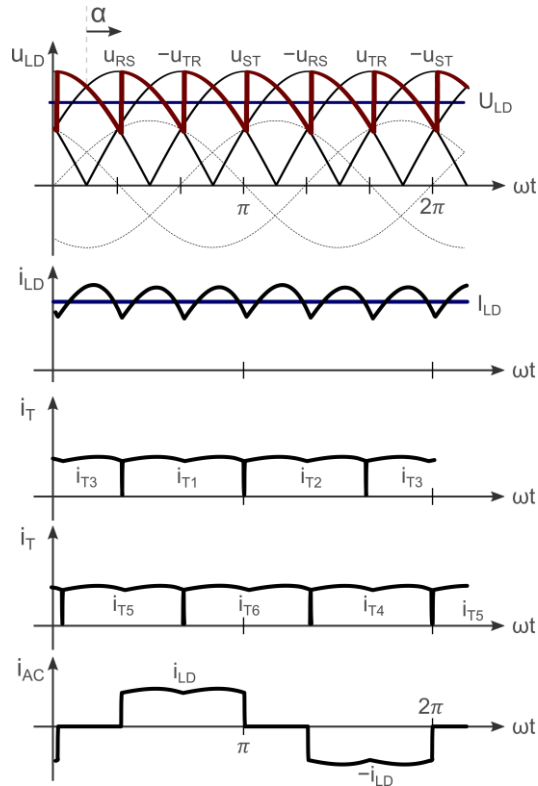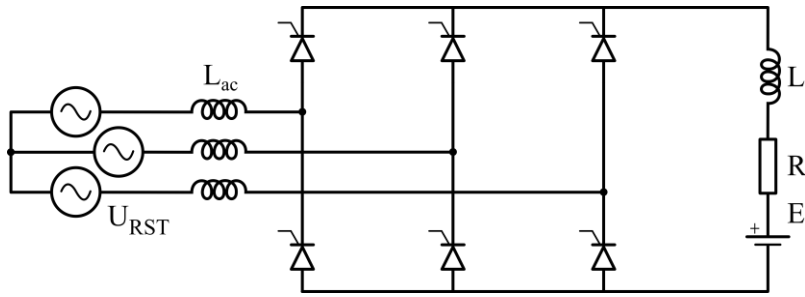
Three-phase thyristor (controlled) rectifier




RECTIFIERS

Three-phase thyristor (controlled) rectifier


Direct start:

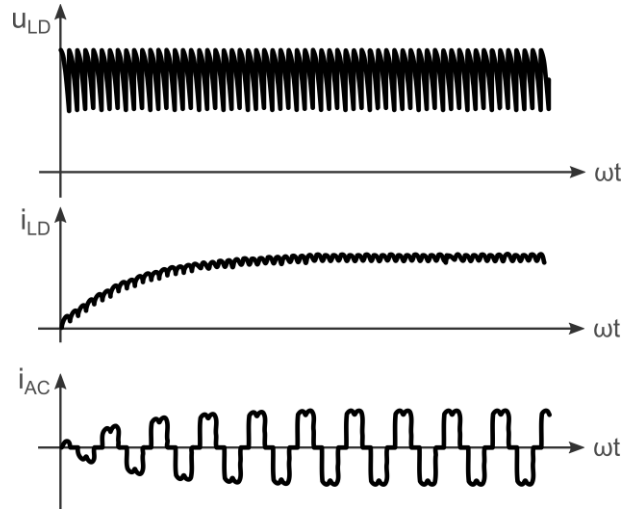

Discontinuous i_{LD} :

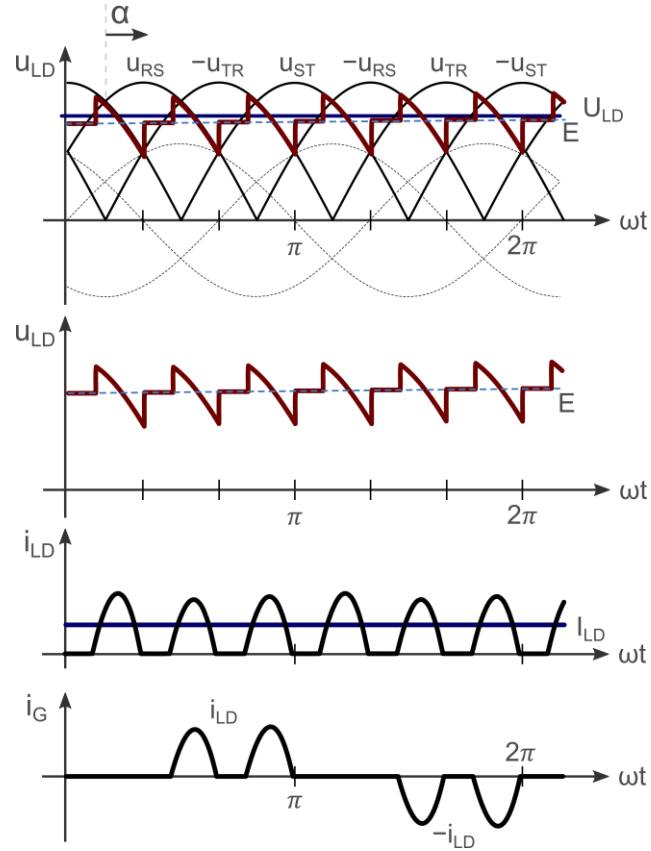


Synchronization:

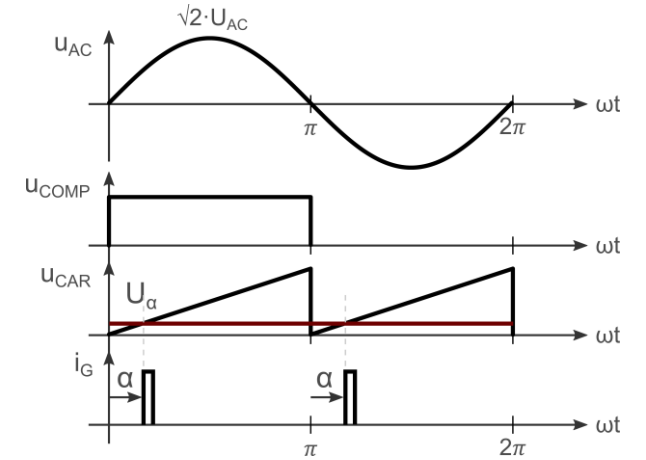

RECTIFIERS



Three-phase thyristor (controlled) rectifier

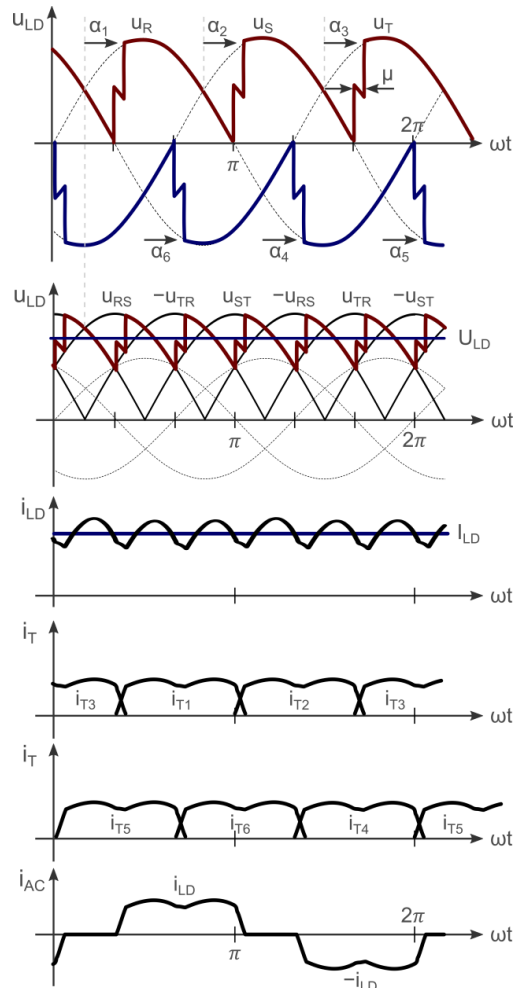Continuous conduction mode
(continuous i_{LD}):



Average load voltage (U_{LD}):


Average load current (I_{LD}):

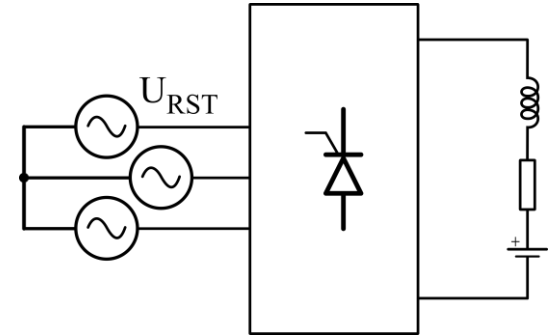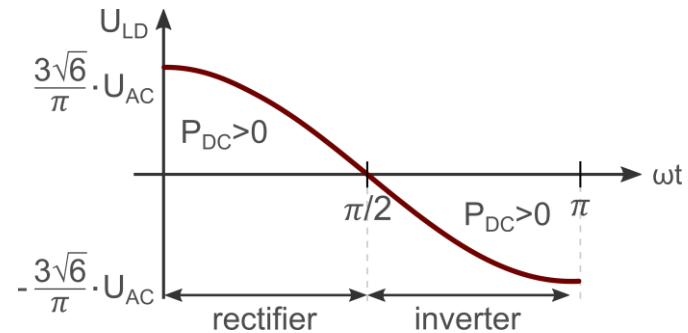

RECTIFIERS

Three-phase thyristor (controlled) rectifier

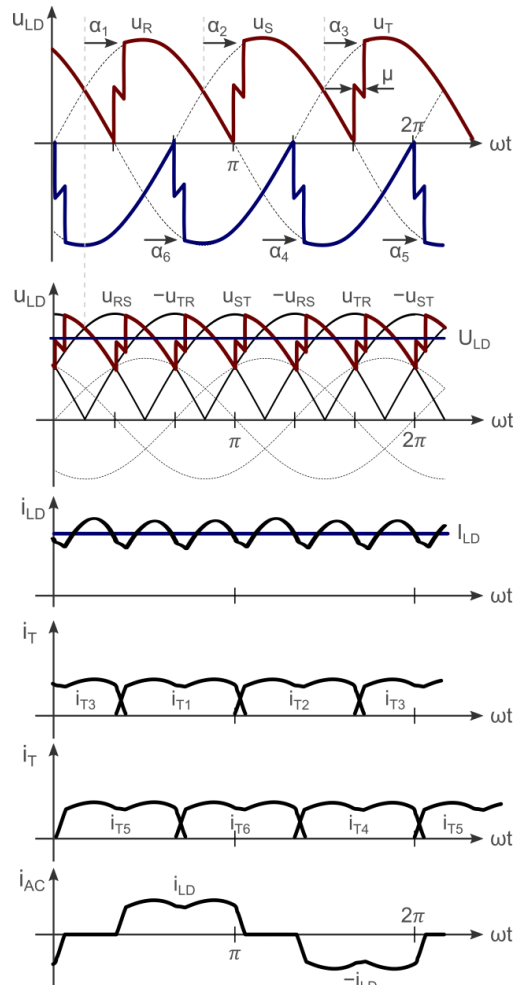Continuous conduction mode
(continuous i_{LD}):



$$U_{AC} = 3 \times 400V \text{ (50Hz)}, R = 1\Omega, L = 30mH, E = 417,8V,$$



$$L_{ac} = 100\mu H, \alpha = \frac{\pi}{6}$$

Average load voltage - example:

$$U_{LD} = \frac{3\sqrt{2}}{\pi} \cdot U_L \cdot \cos\alpha = \frac{3\sqrt{2}}{\pi} \cdot 400 \cdot \cos\left(\frac{\pi}{6}\right) = 467,8V$$

Average load current - example:
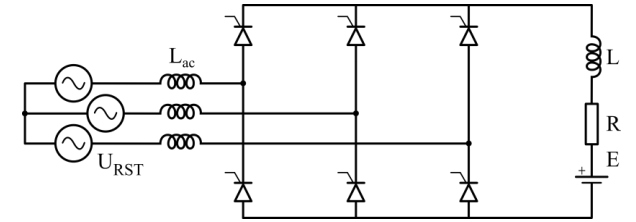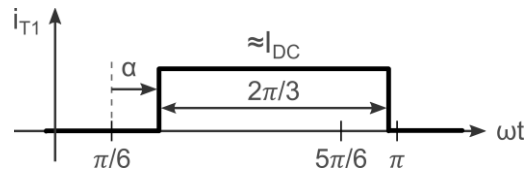
$$I_{LD} = \frac{U_{LD} - E}{R} = \frac{467,8 - 417,8}{1} = 50A$$




Choose thyristors:

RECTIFIERS

Single-phase thyristor (controlled) rectifier

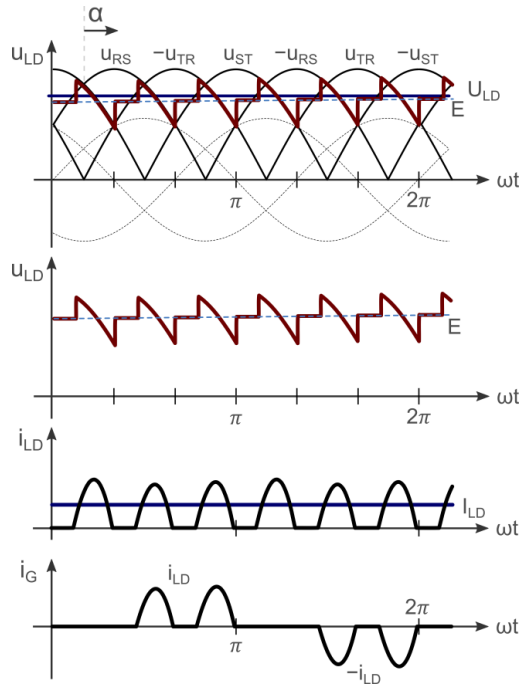Discontinuous conduction mode
(discontinuous i_{LD}):




Average load voltage (U_{LD}):

$$U_{LD} = \frac{1}{\pi/3} \left[\int_{\frac{\pi}{6}+\alpha}^{\frac{\pi}{6}+\beta} \sqrt{2} \cdot U_L \cdot \sin\left(\omega t + \frac{\pi}{6}\right) \cdot d(\omega t) + \int_{\frac{\pi}{6}+\beta}^{\frac{\pi}{2}+\alpha} E \cdot d(\omega t) \right] = \dots$$

Average load current (I_{LD}):

$$I_{LD} = \frac{U_{LD} - E}{R}$$

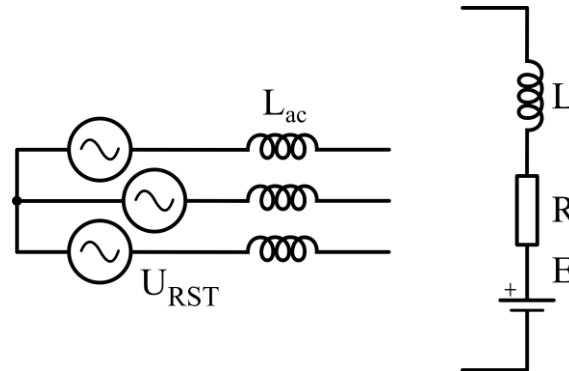

RECTIFIERS

Three-phase rectifiers - important notes

- Three-phase rectifiers are used in higher power applications,
- There are controlled and uncontrolled rectifiers,
- Filtering is extensively used,
- Filters influence the semiconductor devices conduction times,
- Diode bridge secures output voltage with small ripple,
- Thyristor bridge secures output current with small ripple,
- They drive different types of load,
- Load current can be discontinuous in thyristor bridges,
- Thyristor bridges necessitate synchronization unit,
- Commutation is process of importance for thyristor bridges,
- For continuous load current, the thyristor bridge can behave both as a rectifier and as an inverter (depending on firing angle).

